


# CSC 411

## Computer Organization (Fall 2024)

### Lecture 17: Introduction to logic design

**Prof. Marco Alvarez, University of Rhode Island**

## Context

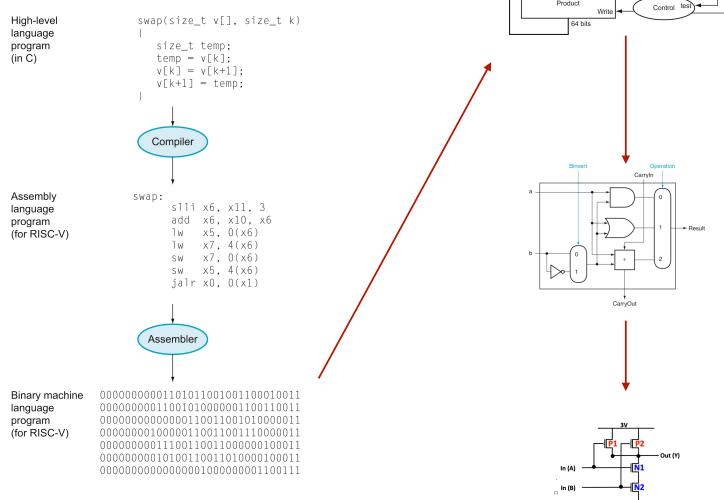


## Disclaimer

Some figures and slides are adapted from:

# Computer Organization and Design (Patterson and Hennessy)

## The Hardware/Software Interface

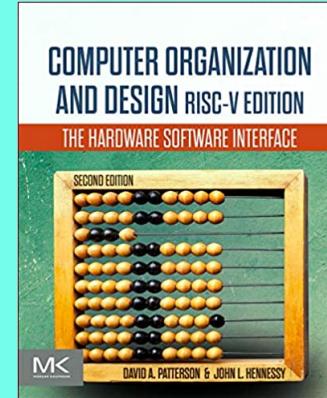

# Circuit design


#### ‣ Key design considerations

- area optimization
  - speed and throughput
  - power and energy efficiency
  - design time and complexity
  - application-specific requirements

# Computing systems today


General Purpose

CPUs

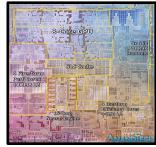


Apple M1

GPUs

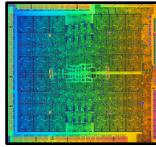

Nvidia GTX 1070


FPGAs

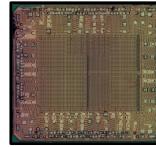

Xilinx Spartan

Special Purpose

ASICs

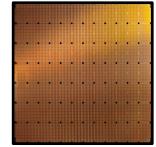

Cerebras WSE-2

Flexible: Can execute any program  
Easy to program & use

Not the best performance & efficiency

Efficient & High performance  
(Usually) Difficult to program & use  
Inflexible: Limited set of programs


All Computers are built upon the same building blocks


Credit: Digital Design & Computer Architecture, Our Mutlu, ETH, 2023

# Transistors

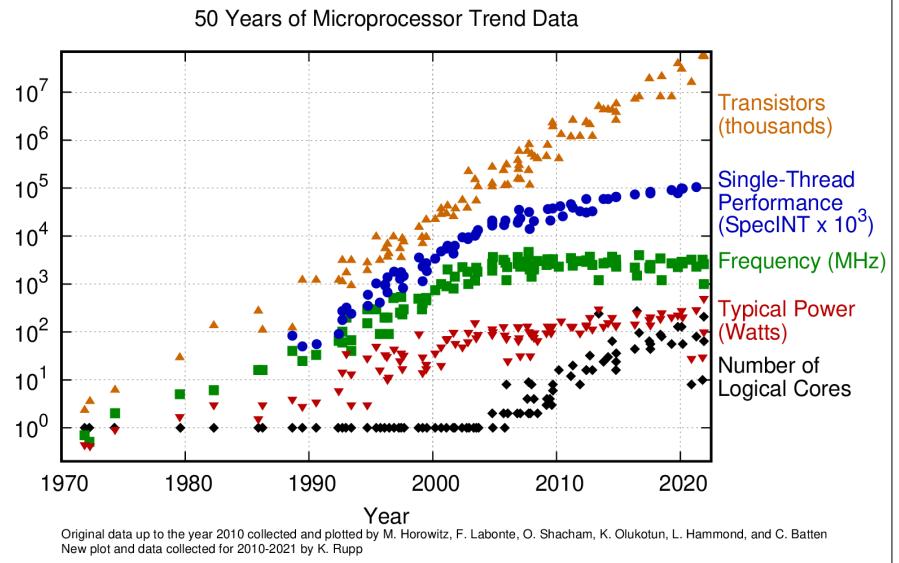
## Moore's Law

- Number of transistors on integrated circuits doubles approximately every 18-24 months
  - Coined by Gordon Moore in 1965, Co-founder of Intel
  - started as an observation, it has been predicated to stop many times
- Currently ...
  - facing physical limitations
  - shift towards architectural innovations




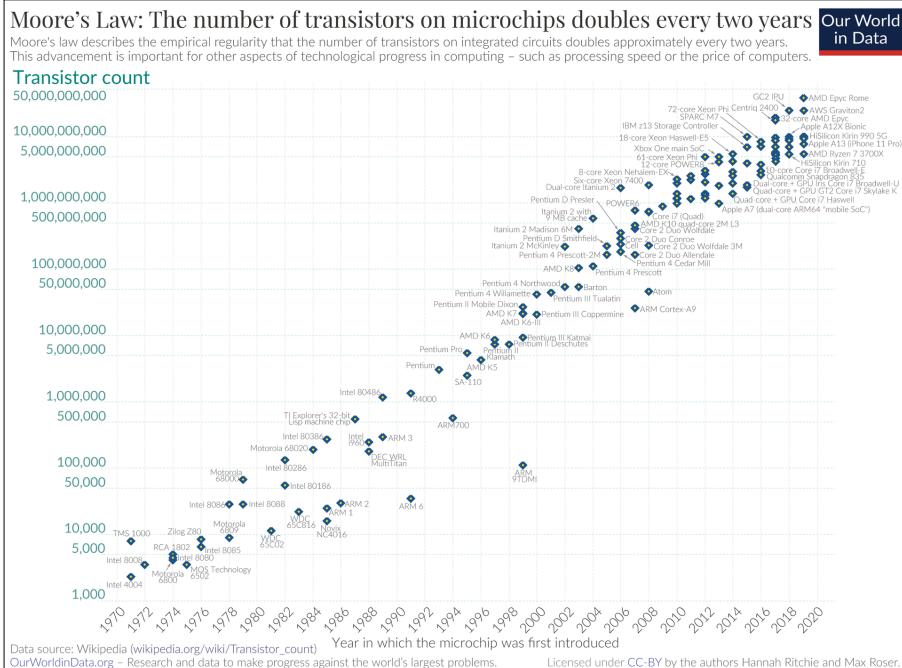

## Apple's M3

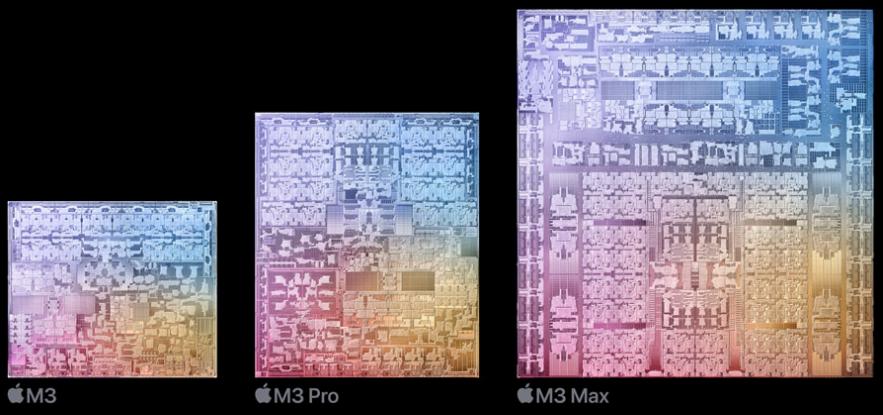

## Apple's M3

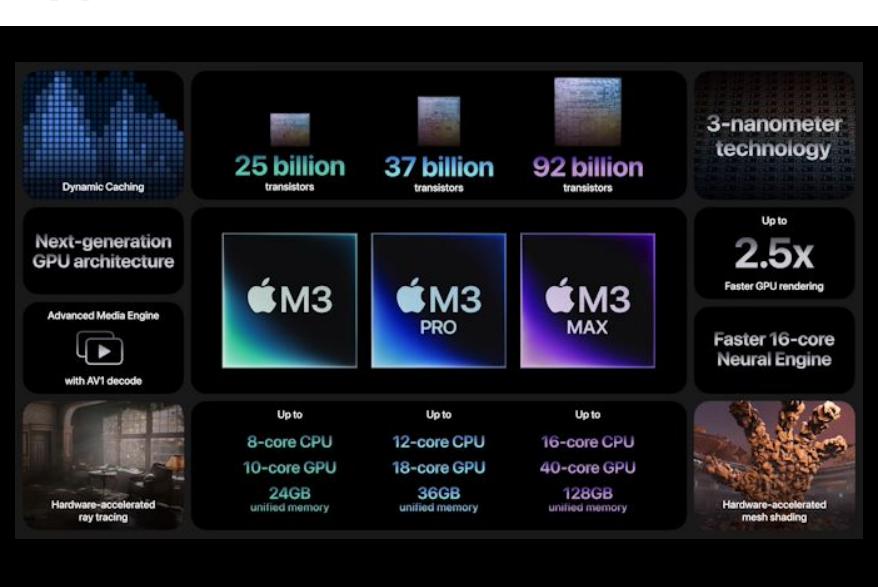


## Transistors

### MOS transistors

- Metal-Oxide-Semiconductor transistors
- **fundamental building block** of computers
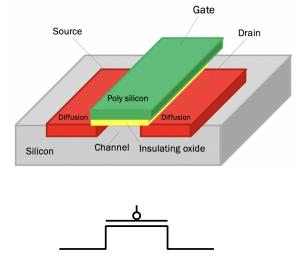
### Components

- **substrate**: semiconductor region that forms the base of the transistor (typically made of silicon)
- **gate**: thin metallic layer insulated from the substrate by a thin layer of oxide
- **source**: a doped region on one side of the substrate where current enters the transistor
- **drain**: a doped region on the other side of the substrate where current exits the transistor
- the type of doping (p-type or n-type) determines whether the transistor is an P-type or N-type transistor



## Switches



conductor  
(closed)



insulator  
(open)


Transistors act as switches and can be combined to implement logic gates

## Types of MOS transistors

### Two types of MOS transistors


- operate as switches

#### n-type

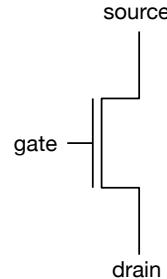

If the gate is supplied with a high voltage, the connection from source to drain acts like a piece of wire

#### p-type

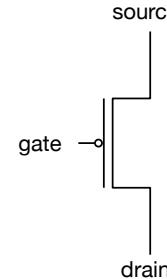

If the gate is supplied with zero voltage, the connection from source to drain acts like a piece of wire

## CMOS technology

### CMOS (complementary MOS)

- combines two types of transistors: **n-type** and **p-type**
- low power consumption, high noise immunity, excellent scalability, high integration densities


### Applications

- CMOS logic gates are used to implement various functional units (e.g., ALU, control unit)
- CMOS technology is used in static RAM (SRAM) and dynamic RAM (DRAM) chips

## Digital logic


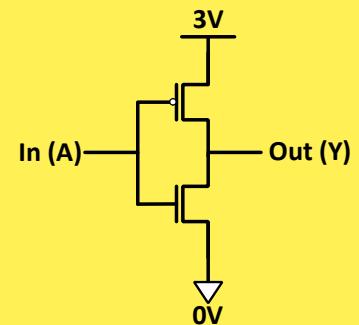
# Logic design basics

- Information encoded in binary (basis of logic design)
  - low voltage, represented as false or 0
  - high voltage, represented as true or 1
  - all other (voltage) values are temporary and occur while transitioning between the low/high voltages
  - use one wire per bit, and multi-wire buses for data that consists of multiple bits (increased data throughput)
- Logic gates
  - implement simple boolean functions
  - can be built using CMOS technology


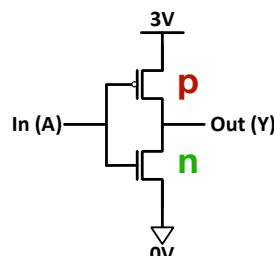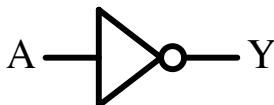
# NOT gate

- The NOT gate is also called an inverter
  - output zero voltage if input is high voltage
  - output high voltage if input is zero voltage



## Truth table

- shows the output for all possible inputs (using binary notation)
- for  $n$  inputs, the truth table contains  $2^n$  entries (all possible combinations of input values)

$$Y = \bar{A}$$

In	Out
0	1
1	0


# Practice

- How many transistors are used?
- What are their types?
- What does this circuit do?

# Practice


- How many transistors are used?
- Complete the truth table
- What does this circuit do?

A	B	P1	P2	N1	N2	Y

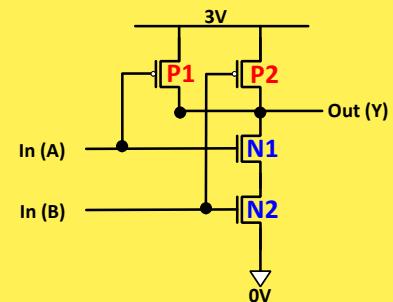
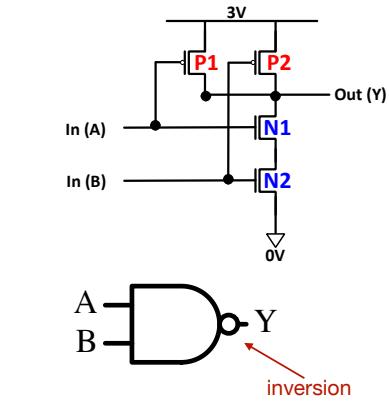
## NAND gate

- P-type transistors in parallel
- only one must be "closed" (conducting) for the output to be high
- N-type transistors connected in series
- both transistors must be "closed" (conducting) to pull the output low




A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

$$Y = \overline{AB}$$
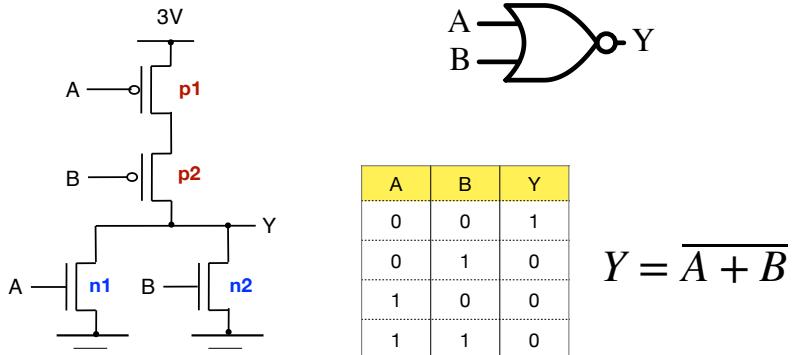
## NOR gate

- P-type transistors are connected in series
- N-type transistors in parallel




A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

$$Y = \overline{A + B}$$

## AND gate

- Combining a NAND gate with a NOT gate

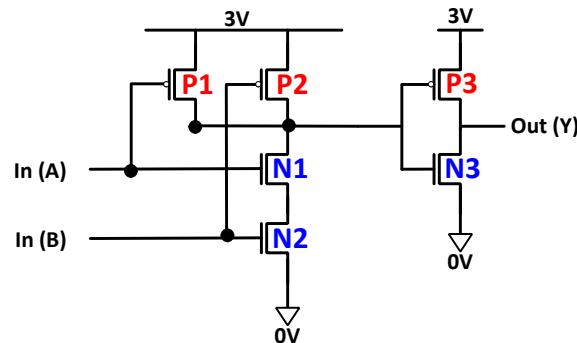


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = AB$$

## Logic gates (notation)

Buffer

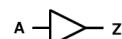

A	Z
0	0
1	1

AND




A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

OR




A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

XOR

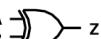

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

Inverter

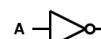


A	Z
0	1
1	0

NAND




A	B	Z
---	---	---

NOR

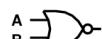

A	B	Z
---	---	---


XNOR

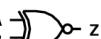

A	B	Z
---	---	---

NAND and NOR are universal. Can implement any boolean function with just NAND or NOR gates.

intel.

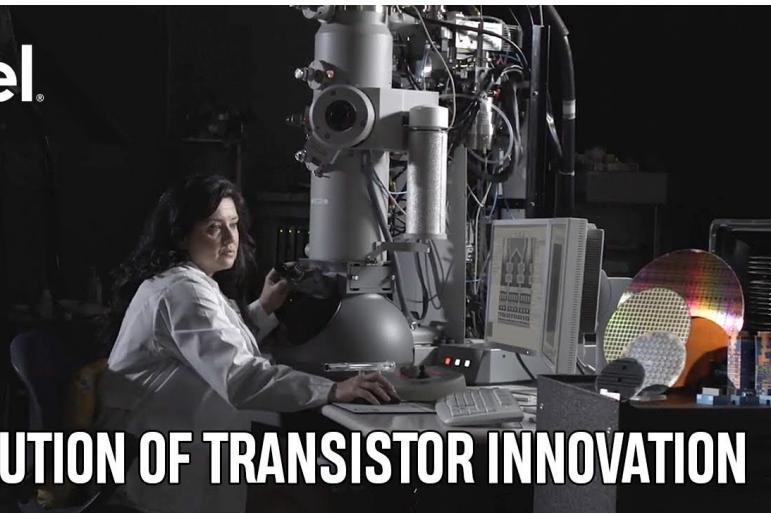

## EVOLUTION OF TRANSISTOR INNOVATION