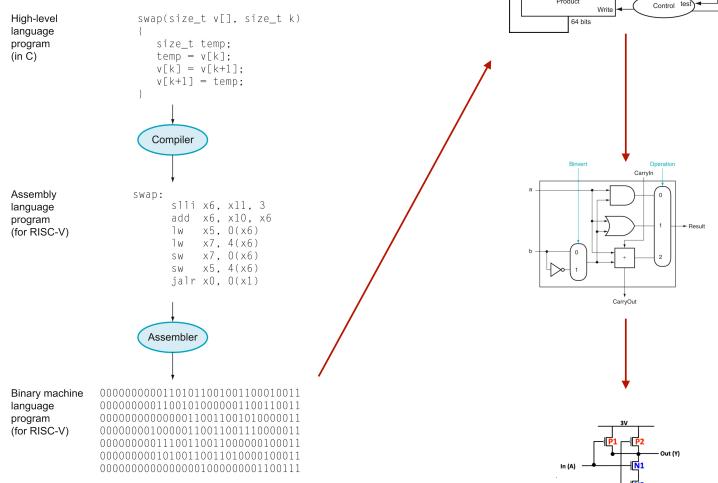


CSC 411

Computer Organization (Fall 2024)
Lecture 17: Introduction to logic design

Prof. Marco Alvarez, University of Rhode Island


Context



Disclaimer

Some figures and slides are adapted from:

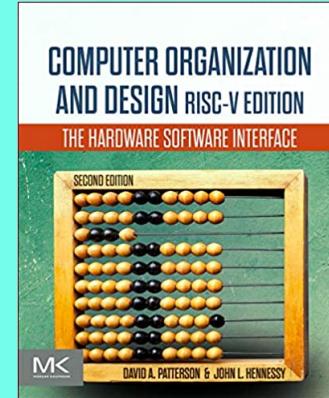Computer Organization and Design (Patterson and Hennessy)
The Hardware/Software Interface




Circuit design

- Key design considerations
 - area optimization
 - speed and throughput
 - power and energy efficiency
 - design time and complexity
 - application-specific requirements

Computing systems today


General Purpose

CPUs

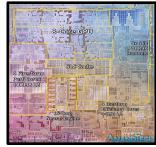


Apple M1

GPUs

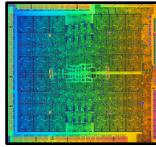

Nvidia GTX 1070


FPGAs

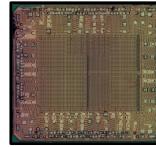

Xilinx Spartan

Special Purpose

ASICs

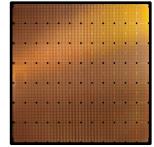

Cerebras WSE-2

Flexible: Can execute any program
Easy to program & use

Not the best performance & efficiency

Efficient & High performance
(Usually) Difficult to program & use
Inflexible: Limited set of programs


All Computers are built upon the same building blocks


Credit: Digital Design & Computer Architecture, Our Mutlu, ETH, 2023

Transistors


Moore's Law

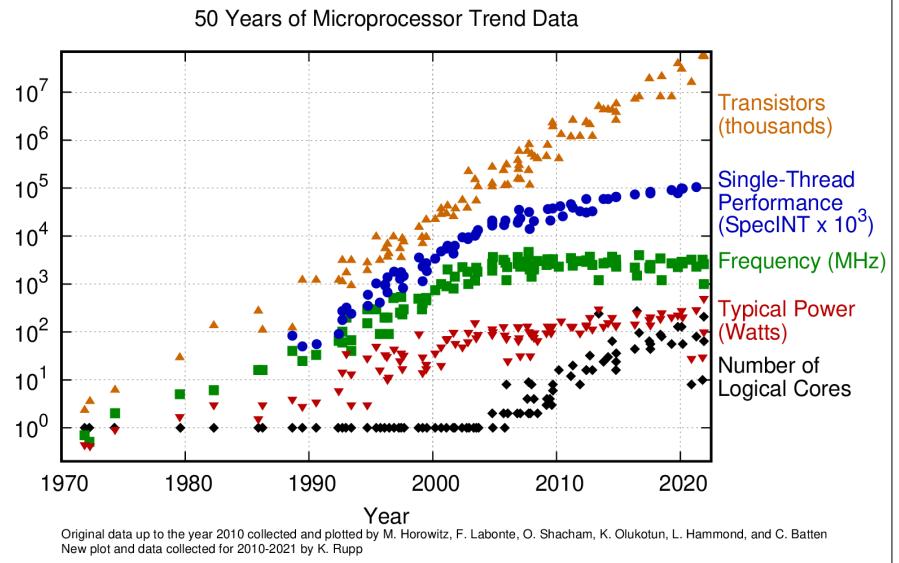- Number of transistors on integrated circuits doubles approximately every 18-24 months
 - Coined by Gordon Moore in 1965, Co-founder of Intel
 - started as an observation, it has been predicated to stop many times
- Currently ...
 - facing physical limitations
 - shift towards architectural innovations



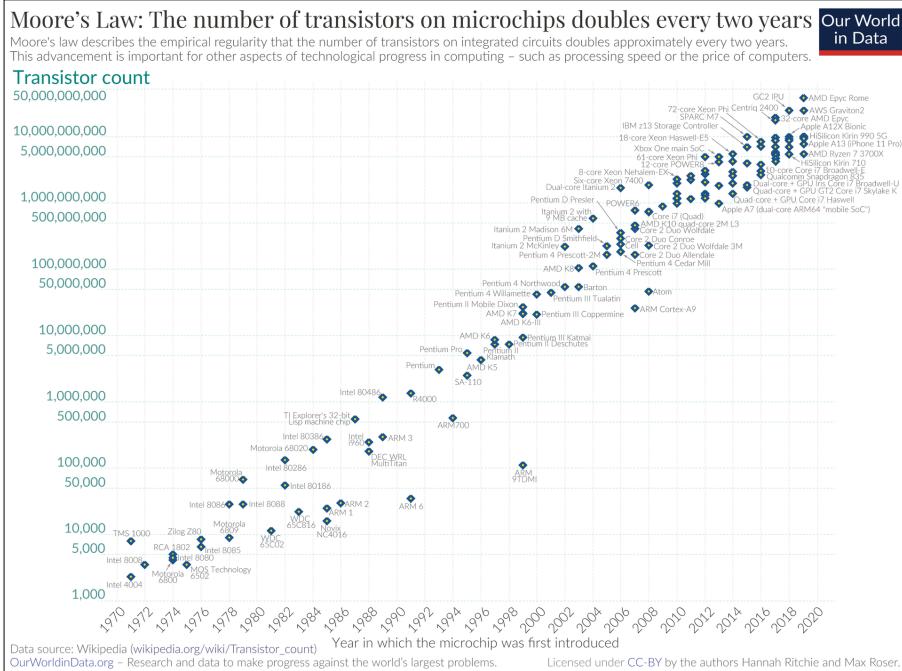

Apple's M3

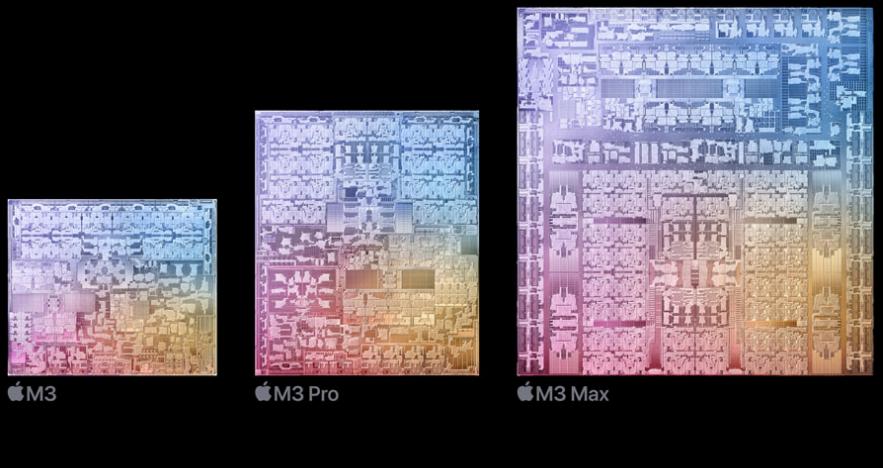

Apple's M3




Transistors

MOS transistors

- Metal-Oxide-Semiconductor transistors
- fundamental building block** of computers

Components

- substrate:** semiconductor region that forms the base of the transistor (typically made of silicon)
- gate:** thin metallic layer insulated from the substrate by a thin layer of oxide
- source:** a doped region on one side of the substrate where current enters the transistor
- drain:** a doped region on the other side of the substrate where current exits the transistor
- the type of doping (p-type or n-type) determines whether the transistor is an P-type or N-type transistor

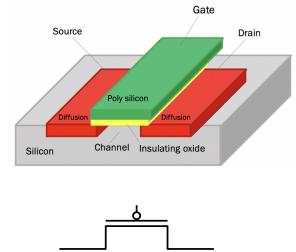

Switches



conductor
(closed)



insulator
(open)


Transistors act as switches and can be combined to implement logic gates

Types of MOS transistors

Two types of MOS transistors


- operate as switches

n-type

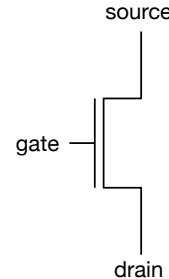

If the gate is supplied with a high voltage, the connection from source to drain acts like a piece of wire

p-type

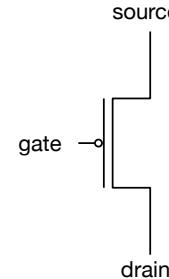

If the gate is supplied with zero voltage, the connection from source to drain acts like a piece of wire


CMOS technology

- CMOS (complementary MOS)
 - combines two types of transistors: **n-type** and **p-type**
 - low power consumption, high noise immunity, excellent scalability, high integration densities
- Applications
 - CMOS logic gates are used to implement various functional units (e.g., ALU, control unit)
 - CMOS technology is used in static RAM (SRAM) and dynamic RAM (DRAM) chips

Digital logic



Logic design basics

- Information encoded in binary (basis of logic design)
 - low voltage, represented as false or 0
 - high voltage, represented as true or 1
 - all other (voltage) values are temporary and occur while transitioning between the low/high voltages
 - use one wire per bit, and multi-wire buses for data that consists of multiple bits (increased data throughput)
- Logic gates
 - implement simple boolean functions
 - can be built using CMOS technology

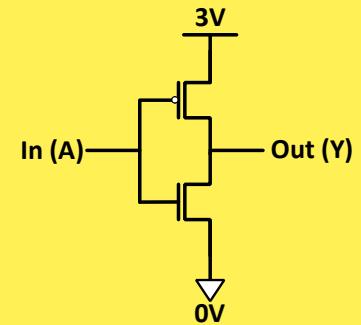

NOT gate

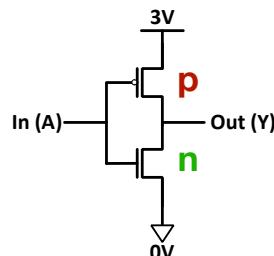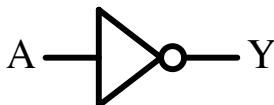- The NOT gate is also called an inverter
 - output zero voltage if input is high voltage
 - output high voltage if input is zero voltage



Truth table

- shows the output for all possible inputs (using binary notation)
- for n inputs, the truth table contains 2^n entries (all possible combinations of input values)

$$Y = \bar{A}$$

In	Out
0	1
1	0


Practice

- How many transistors are used?
- What are their types?
- What does this circuit do?

Practice


- How many transistors are used?
- Complete the truth table
- What does this circuit do?

A	B	P1	P2	N1	N2	Y

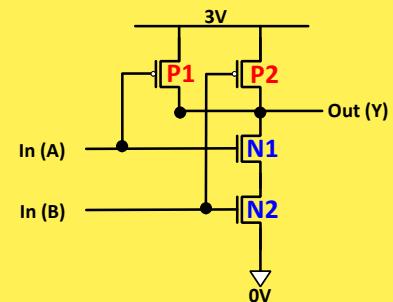


NAND gate

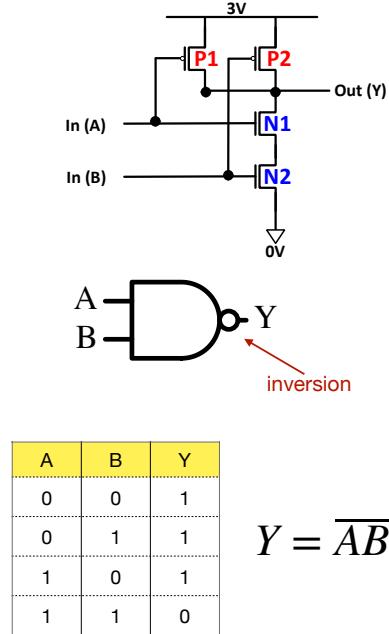- P-type transistors in parallel
- only one must be "closed" (conducting) for the output to be high
- N-type transistors connected in series
- both transistors must be "closed" (conducting) to pull the output low




NOR gate

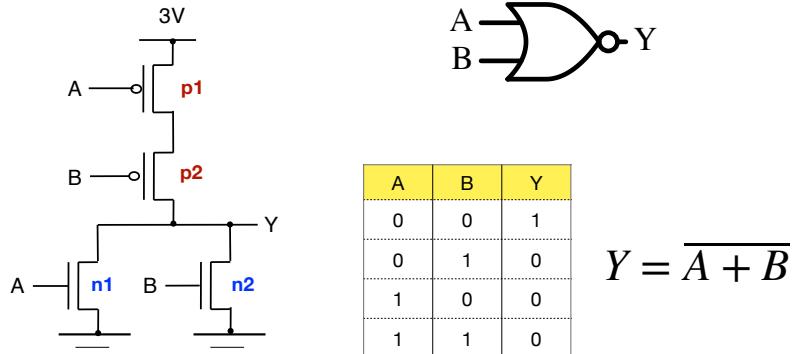- P-type transistors are connected in series
- N-type transistors in parallel



AND gate

- Combining a NAND gate with a NOT gate

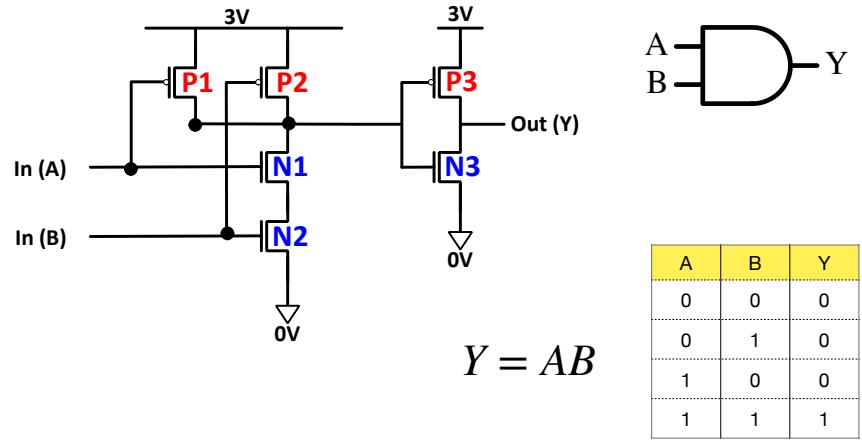


Logic gates (notation)

Buffer	AND	OR	XOR
Inputs	Inputs	Inputs	Inputs
A Z	A B Z	A B Z	A B Z
0 0	0 0 0	0 0 0	0 0 0
1 1	0 1 0	0 1 1	0 1 1

NAND and NOR are universal. Can implement any boolean function with just NAND or NOR gates.

intel.

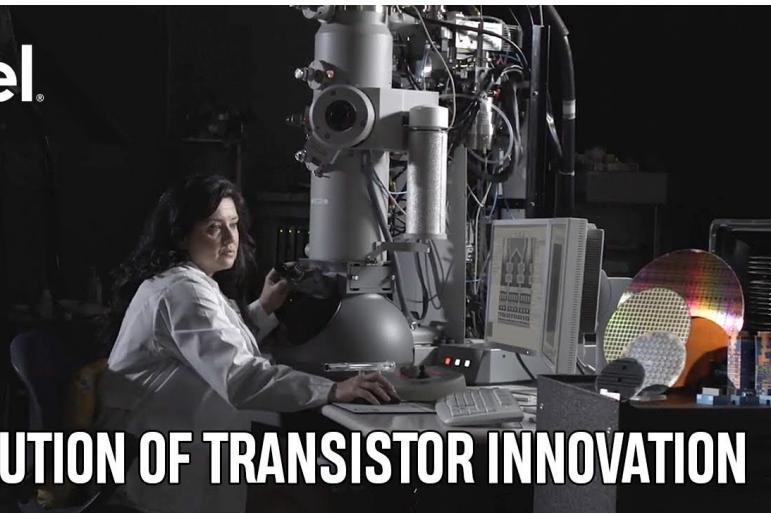

EVOLUTION OF TRANSISTOR INNOVATION